

Name: _____

Class: _____

Date: _____

Mr. Rawson • GCSE Physics

REVIEW — Series Resistors

Keep this sheet. Everything you need for series circuits is on this side.

Key concept

THE THREE RULES — series (one loop, no choice of route)

1. **Current is the same everywhere.** $I_1 = I_2 = I_{\text{supply}}$

Charge is not used up. An ammeter reads the same wherever you put it in the loop.


2. **Potential difference is shared out.** $V_{\text{supply}} = V_1 + V_2$

The bigger resistor takes the bigger share.

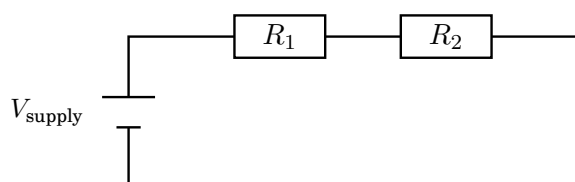3. **Resistances add.** $R_{\text{total}} = R_1 + R_2$

Adding a resistor in series always *increases* total resistance — the charge must pass through every one of them, so there is more opposition on the single route available.

And $V = IR$ still applies to *every single component*, as well as to the whole circuit.



same current all the way round

Worked example

WORKED EXAMPLE 1 — the standard one

A $4\ \Omega$ and a $6\ \Omega$ resistor are connected in series to a $12\ \text{V}$ supply. Find the current, and the potential difference across each resistor.

1. **Total resistance** $R_{\text{total}} = R_1 + R_2 = 4 + 6 = 10\ \Omega$
2. **Current** $I = \frac{V}{R} = \frac{12}{10} = 1.2\ \text{A}$ (this is the current *everywhere*)
3. **Each p.d.** $V_1 = IR_1 = 1.2 \times 4 = 4.8\ \text{V}$
 $V_2 = IR_2 = 1.2 \times 6 = 7.2\ \text{V}$
4. **Check** $4.8 + 7.2 = 12\ \text{V}$ ✓ matches the supply — rule 2

Worked example

WORKED EXAMPLE 2 — working backwards

A $9\ \text{V}$ supply drives a current of $0.30\ \text{A}$ through two resistors in series. One of them is $12\ \Omega$. Find the other.

1. **Total resistance** $R_{\text{total}} = \frac{V}{I} = \frac{9}{0.30} = 30\ \Omega$
2. **Subtract** $R_2 = R_{\text{total}} - R_1 = 30 - 12 = 18\ \Omega$

Name: _____

Date: _____

REVIEW — Series Resistors: practice

1) **State** what happens to the size of the current as you move an ammeter to different points around a series circuit. [1]

2) **Calculate** the total resistance of a $3\ \Omega$ and a $7\ \Omega$ resistor in series. [1]

3) **Calculate** the current when those two resistors are connected to a $20\ \text{V}$ supply. [2]

4) **Calculate** the potential difference across each of the two resistors. [2]

5) **Show** that your two answers above are consistent with the supply potential difference. [1]

6) **Calculate** the unknown resistance: a $12\ \text{V}$ supply drives $0.40\ \text{A}$ through two resistors in series, one of which is $10\ \Omega$. [3]

7) **Explain** qualitatively why adding another resistor in series *increases* the total resistance of a circuit. [2]

8) **Explain** what happens to the other lamp when one lamp in a series circuit is removed, and why. [2]