



Name: _____
Class: _____
Date: _____

Mr. Rawson • GCSE Physics

RP 16: I-V Characteristics

Key concept — Ohm's law

$$V = I R \quad \text{potential difference (V) = current (A) } \times \text{ resistance } (\Omega)$$

Rearranged to find the resistance:

$$R = \frac{V}{I}$$

Two weeks ago you measured how resistance changes with the length of a nichrome wire and you got a **straight line**, showing a linear relationship. The wire followed Ohm's Law directly.

Today's question is testing if other components also follow Ohm's Law. Some components don't always follow the linear relationship between current and voltage like a wire does. As you push more current through certain devices, some devices change their resistance.

Reading an I-V graph (this is the whole skill)

You are plotting **current** on the y -axis against **potential difference** on the x -axis.

- If the I-V graph is a **Straight line** through the origin $\rightarrow$ a **linear relationship**. This shows the resistance is **constant**: doubling V doubles I .
- If the I-V graph is a **Curved line** $\rightarrow$ the component does **not** follow Ohm's law. $R = V/I$ still gives the resistance at each point, but that resistance is changing.

Test the positive AND the negative You will reverse the direction of the current flow, and take readings with the pd the other way round so you can plot points along the positive and negative axes.


The question

How do the I-V characteristics change for different components in a circuit? Which ones follow Ohm's Law?

You will test **three components**: a fixed resistor, a filament lamp, and a diode.

Independent variable what you change	
Dependent variable what you measure	
Control variables what stays the same	

The circuit

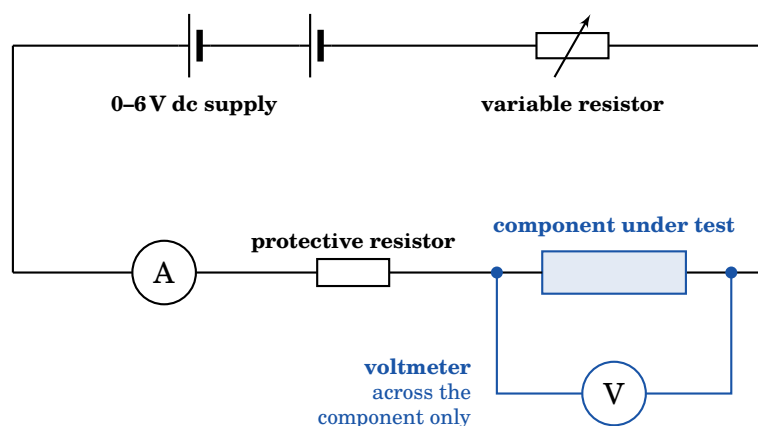

One circuit, three components. You build it once and swap only the blue box. The supply sets the big steps; the variable resistor sets the small steps in between. For the top of the range, turn it to its lowest resistance. The ammeter is in the loop, so the whole current goes through it. The voltmeter goes across the component alone.

Remember your Ammeter and Voltmeter Rules


- The Ammeter must be placed **in series** with the rest of the circuit. An ideal ammeter has **zero resistance** so it does not affect the resistance in series.
- The Voltmeter must be placed **in parallel** with the rest of the circuit. An ideal voltmeter has **infinite resistance** so it will stop any current flow if it is placed in series.

Method

1. Build the circuit above with the **fixed resistor** as the component under test. Leave the supply **off** until you have been checked.
2. Set the supply to its **lowest** setting and turn it on. Read the **voltmeter** and the **ammeter** together, then **turn the supply off again**.
3. Work up through the supply settings, taking a pair of readings at each. Six or seven pairs is plenty. **Turn the supply off between every reading**.
4. **Now reverse**. Switch off, swap the two leads at the supply, and repeat the whole set. Record these readings as **negative** — both the pd and the current.
5. **Plot as you go**, straight onto the grids on the next pages. Do not wait until the end. The shape is the result, and you want to see it appearing.
6. Swap the component for the **filament lamp** and repeat steps 2–5.
7. Swap the component for the **diode** and repeat steps 2–5. Read the box on the diode page **before** you start it.

Component 1 — the fixed resistor

pd V / V	Current I / A	pd V / V	Current I / A
forward		reversed (negative)	

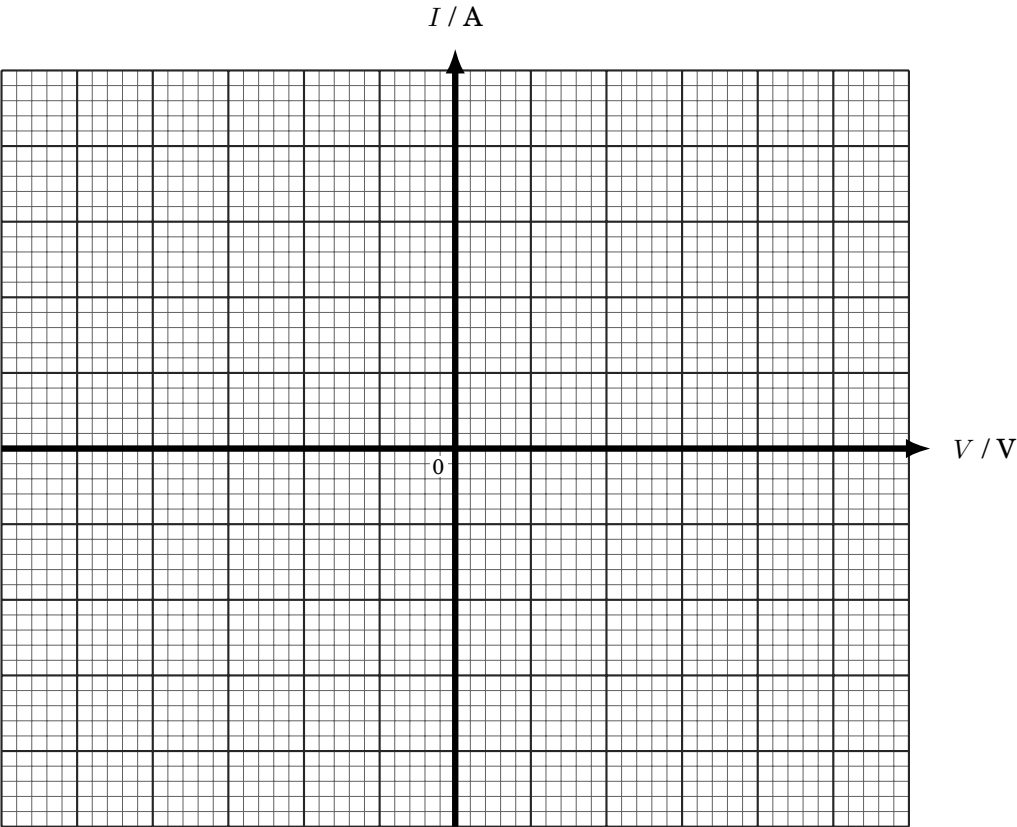


*Label your own scale on both axes first — negative to the left of zero and below it. Then plot every point, forward and reversed, and draw **one** straight line through them all.*

1) **Describe** the shape of your graph.

2) **State** what that shape tells you about the resistance of the fixed resistor.

Component 2 — the filament lamp

pd V / V	Current I / A	pd V / V	Current I / A
forward		reversed (negative)	

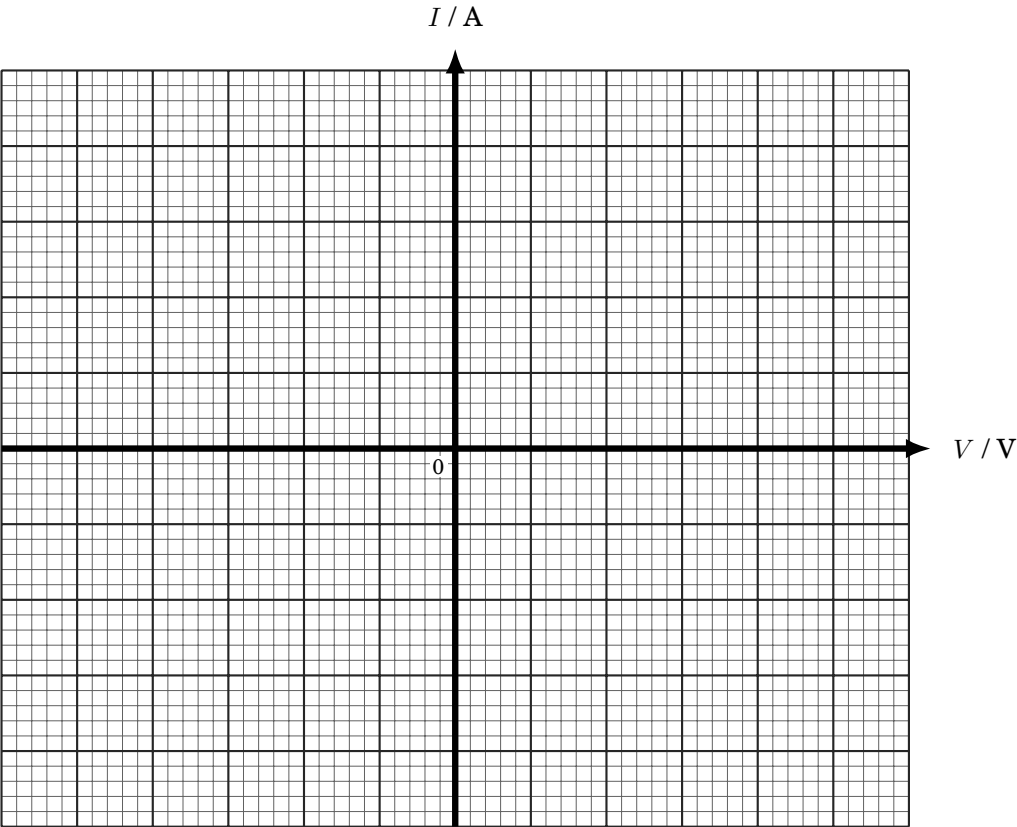

Label your own scale on both axes first. Then plot every point and draw a **smooth curve** — not a straight line, and not dot-to-dot.

3) **Describe** the shape of your graph, and say how it differs from the resistor's.

4) **Explain** why the curve gets flatter as the potential difference increases. Your answer must mention temperature.

5) **Explain** why the curve has the same shape on both sides of the origin.

Component 3 — the diode

Read this before you connect the diode


One way round, you will get a current. The other way round, you will get nothing — and nothing is the correct result.

Do not call it a broken circuit, do not go looking for a loose lead, and do not ask for a new diode. A reading of zero with several volts across it is exactly what a diode is *for*. Write the zeros down: they are your data.

Two further things you will notice in the forward direction:

- Almost nothing happens until about **0.6 V**. Below that the diode barely conducts at all.
- Once it passes that point the current climbs very steeply. **Go up in small steps here** or you will get two useful points and a mess.

pd V / V	Current I / A	pd V / V	Current I / A
forward		reversed (negative)	

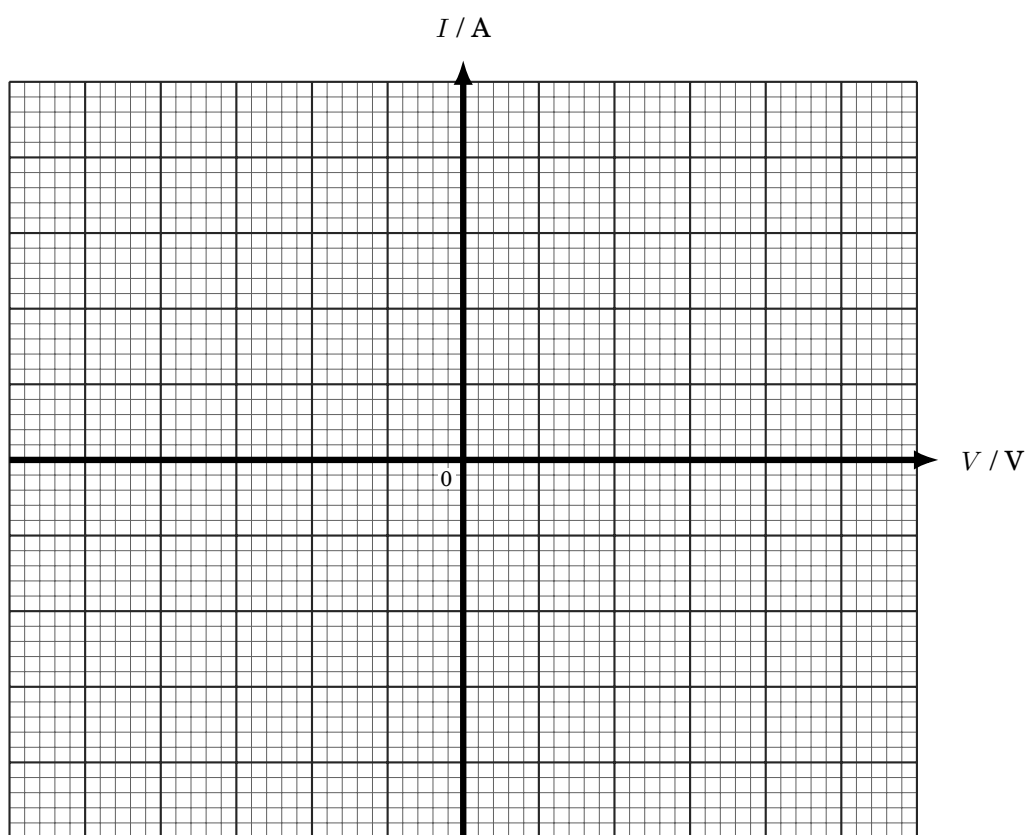

Label your own scale on both axes first. The two halves of this graph do **not** match — draw what you measured, not what looks tidy.

6) **Describe** what your graph does when the potential difference is reversed.

7) **State** what this tells you about the resistance of a diode in the reverse direction.

8) **Complete** the sentence. Circle one: **current through a diode flows** _____.

equally in both directions

in one direction only

only above 6 volts

only when it is hot

9) **Suggest** one job a diode could usefully do in a circuit, given what you have just measured.

Two more components — no practical needed

Your graphs cover the three components AQA names. Two others change their resistance too, and you need to know what changes it.


Component	What changes its resistance	What it is used for
Thermistor		
LDR light-dependent resistor		

The pattern worth spotting. A fixed resistor has one resistance and keeps it. Every other component on this sheet has a resistance that *depends on something* — the current through it, its temperature, or the light falling on it.


Pulling it together

10) **Name** the one component you tested whose resistance stayed constant, and say how the graph showed it.

 
11) **Sketch** all three characteristics side by side, from memory, in the boxes below. Axes only — no numbers.



Fixed resistor

 

Filament lamp

 

Diode

Evaluation

12) **Explain** why the readings for the fixed resistor would be wrong if you left the supply on for the whole experiment.

13) **Give** one reason why the filament lamp's graph is a curve while the fixed resistor's is a straight line, even though both are just pieces of metal wire.

14) **Suggest** one improvement to the method that would make the diode's turn-on point easier to identify.

Extra space for working

A second attempt at a graph, a repeated set of readings, anything that did not fit.

Before you pack away: switch off at the supply, disconnect, and check the lamp is *cool* before it goes back in the tray. Diodes back in their own box — they are easy to lose and easy to destroy. Meters back the way you found them.