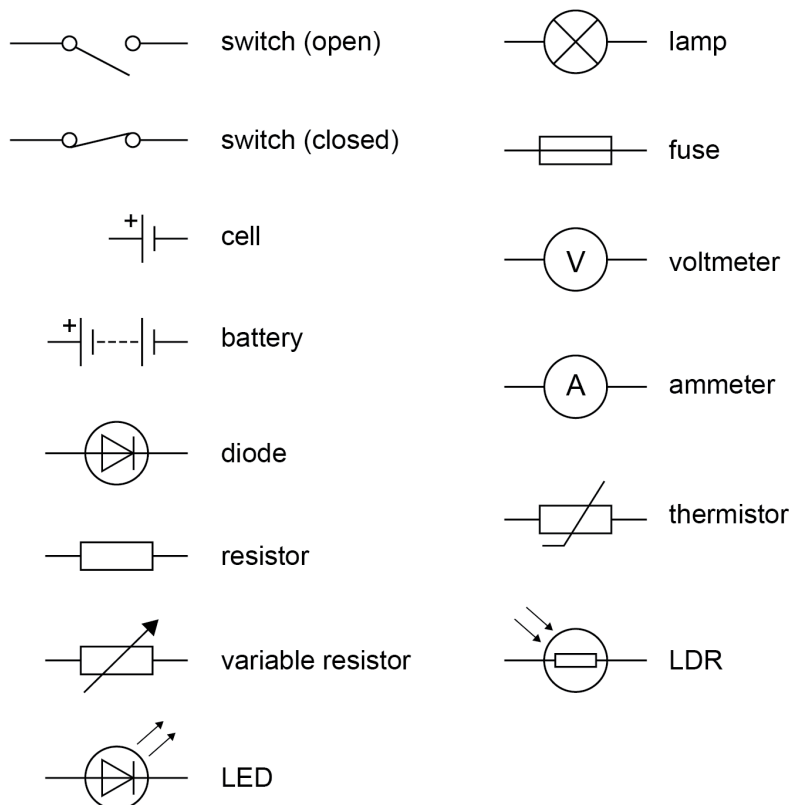


Name: _____
Class: _____
Date: _____

Mr. Rawson • GCSE Physics

REFERENCE — Circuit Symbols

Keep this sheet. These fourteen are the complete list — AQA does not ask you for any others.
The spec says you must be able to **draw** them and **interpret** them. Both are examined.



Reproduced from the AQA GCSE Combined Science: Trilogy (8464) specification, page 128.

Key concept

THREE DETAILS TO GET RIGHT WHEN YOU DRAW THEM

1. **The cell and the battery carry a + —** it marks the positive terminal, which is the *long thin line*.
2. **A battery is two cells with a dashed gap** — not one long cell. The dashes mean “and however many more”.
3. **The LED’s arrows point away; the LDR’s point towards.** The LED *gives out* light, the LDR *responds to* it. Same two arrows, opposite meaning — reverse them and you have drawn the other component.

Key concept

THE THREE WHOSE RESISTANCE IS NOT FIXED (you meet these again in 6.2.1.4)

Variable resistor set by *hand* you slide it to choose the resistance

Thermistor responds to *temperature* resistance *falls* as it gets hotter

LDR responds to *light* resistance *falls* as it gets brighter

The thermistor and the LDR both go *down* in resistance when you give them more of what they respond to. More light, less resistance — that is the one people get backwards.